

# Digital System Design

CE 325 L1  
SPRING 2024

Instructor : Dr. Syed Arsalan Jawed

Associate Professor of Practice

[arsalan.jawed@sse.habib.edu.pk](mailto:arsalan.jawed@sse.habib.edu.pk)

Room : W-301

Office Hours : Monday 0930-1030, Wednesday 1430-1530, Friday 0930-1030


Complement these with the hand-written notes and explanations during the class on the white board!

# Contents of this Lecture


- Digital Design Architecting and Partitioning
  - Computer Architectures and Organization Evolution - briefly
  - Processing Elements / Storage Elements / Interconnection Topologies
  - Upcoming architecture of In-Memory Compute
  - Functional Components inside the Processing Element
    - Datapaths
    - Controllers
- The concept of Register-Transfer-Logic
  - Going from one DFF to the other – through a certain logic cloud
  - Partitioning between Combinational and Sequential logic
- Combinational Logic main functional components and methodologies
  - Static CMOS Logic Family for Gate Design
  - Timing, Area and Power Concepts

# Conventional Computer Architecture

## Von Neumann Architecture Diagram

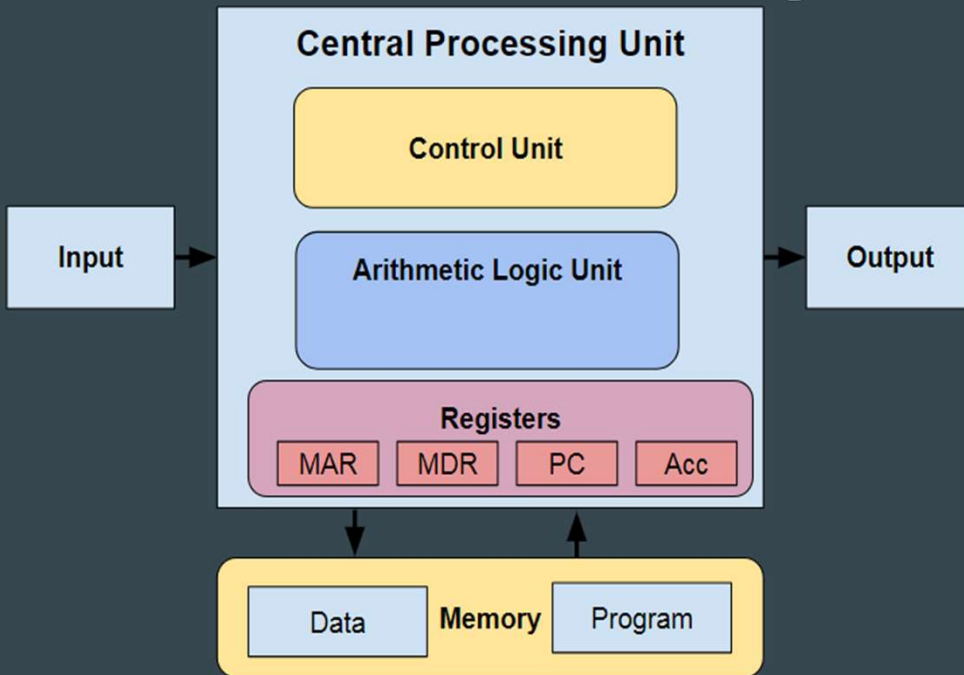


## Von Neumann Vs Harvard Architecture

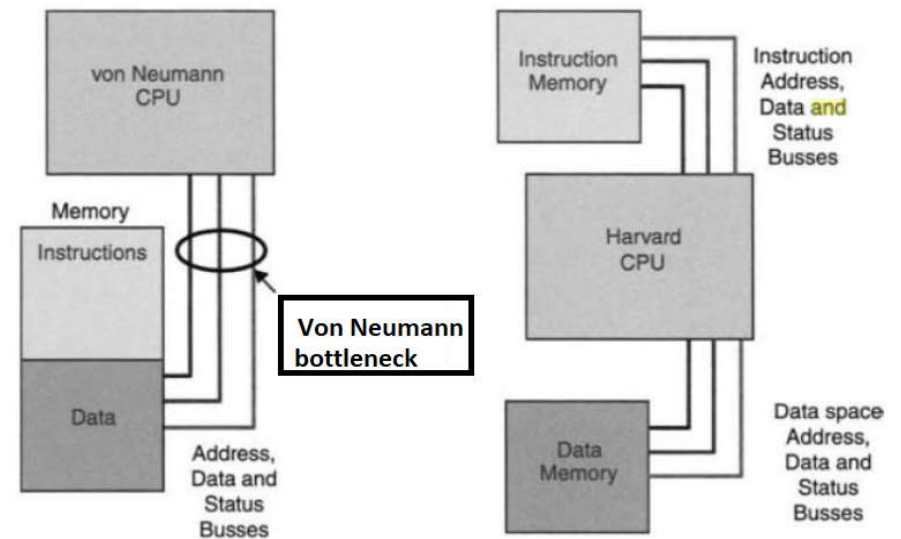


[www.eevibes.com](http://www.eevibes.com)
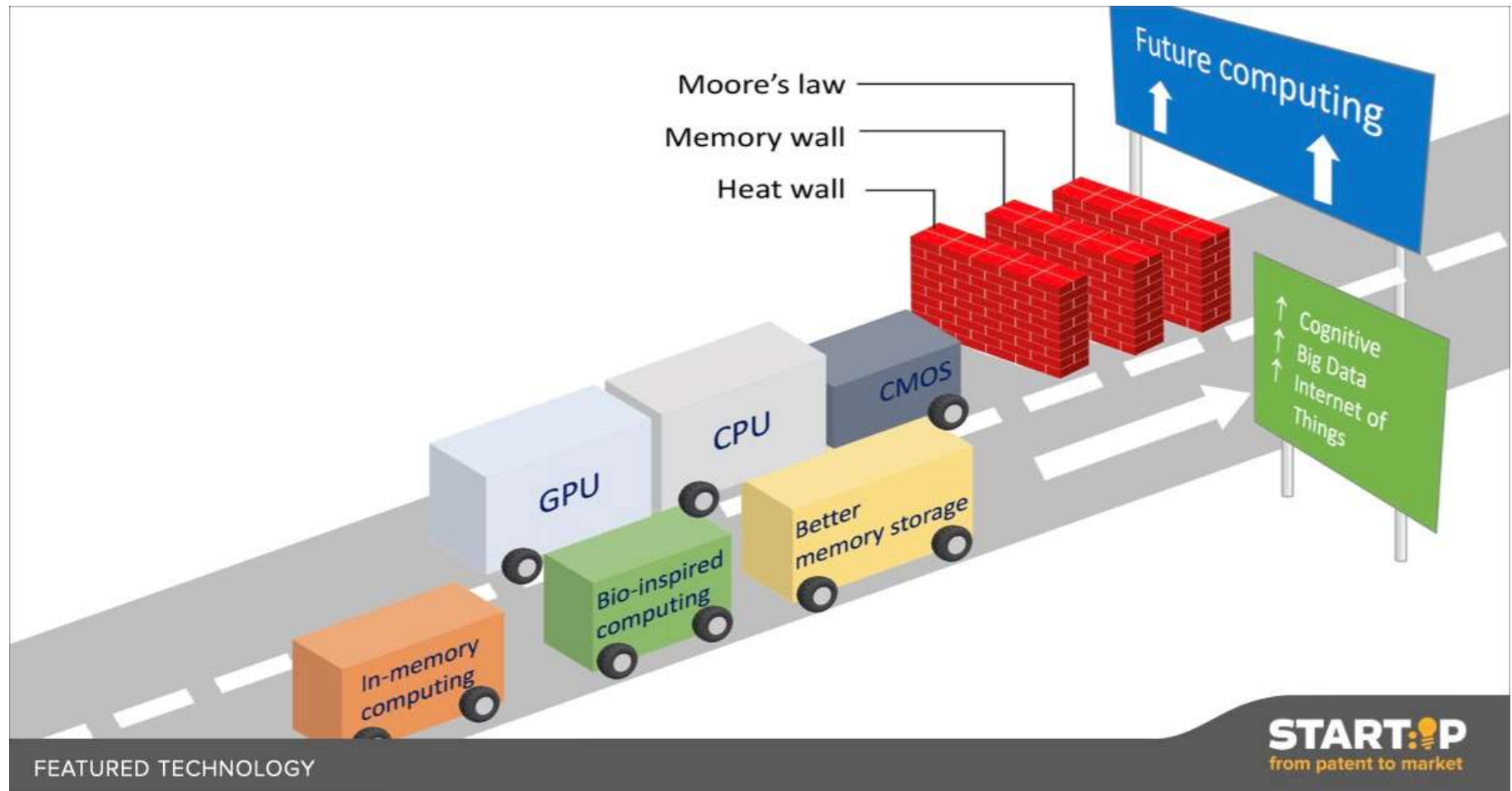
# Emerging Dynamic of Digital Computing Systems





# Upcoming In-Memory Compute

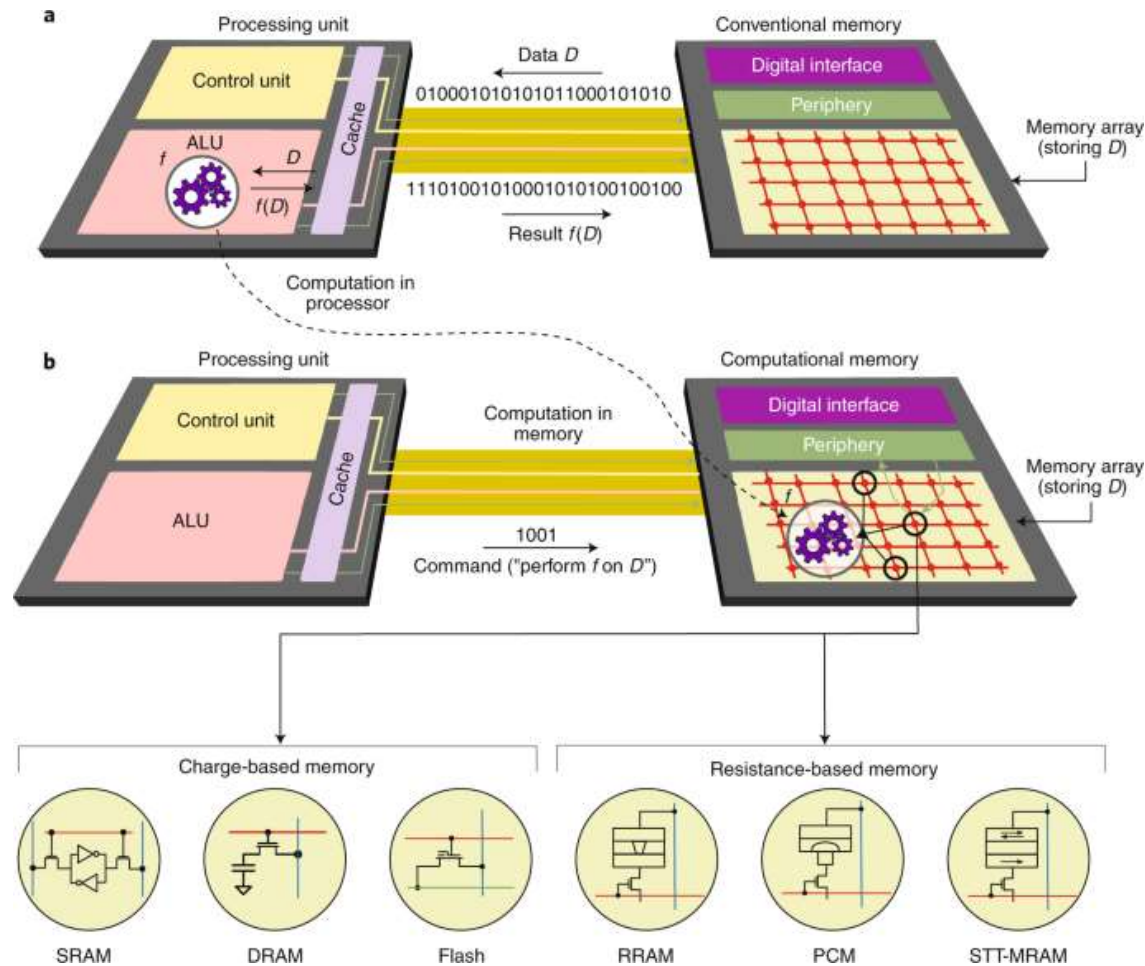

# Neuromorphic Computing

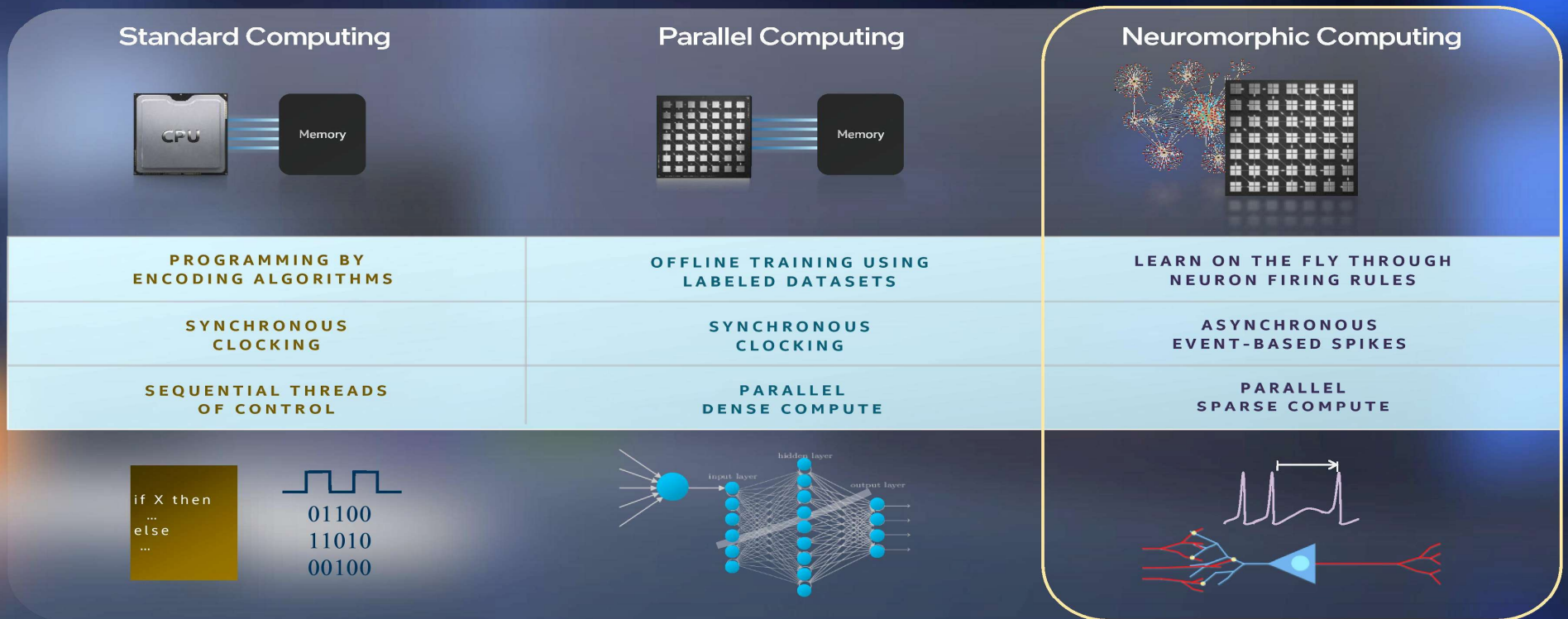
## Motivates a New Kind of Computer Architecture



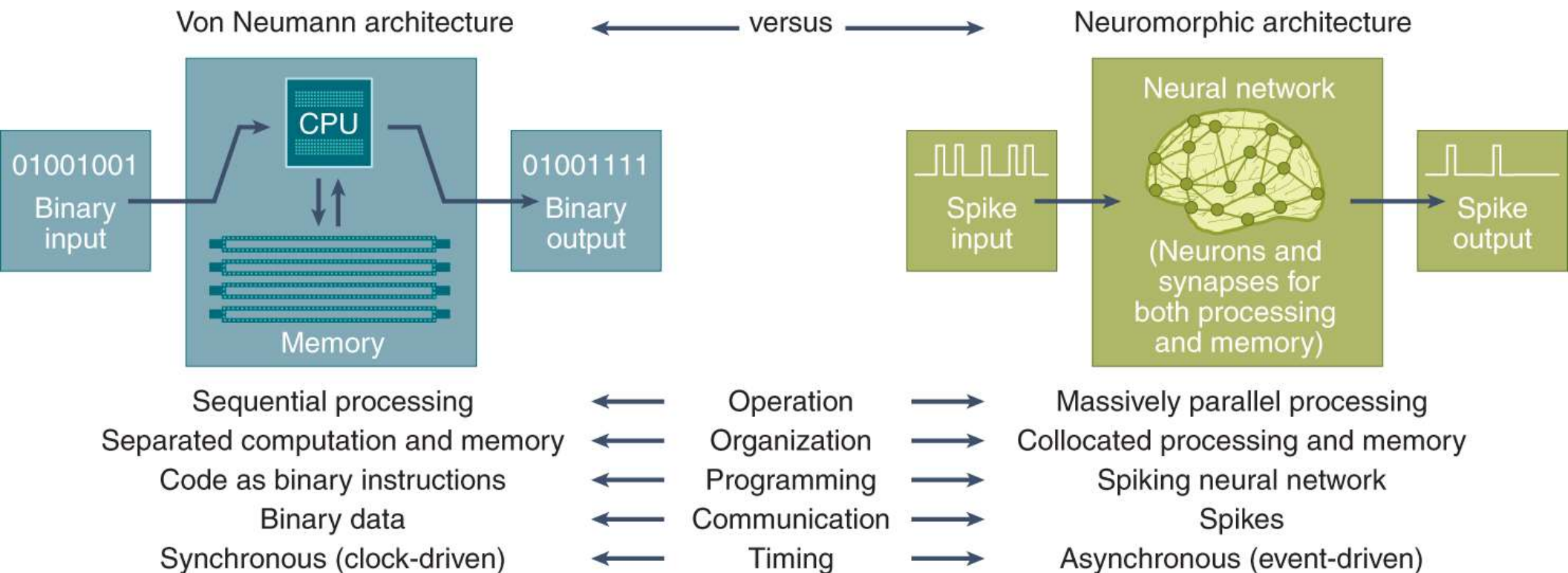




# RISC-V Open Source Architecture

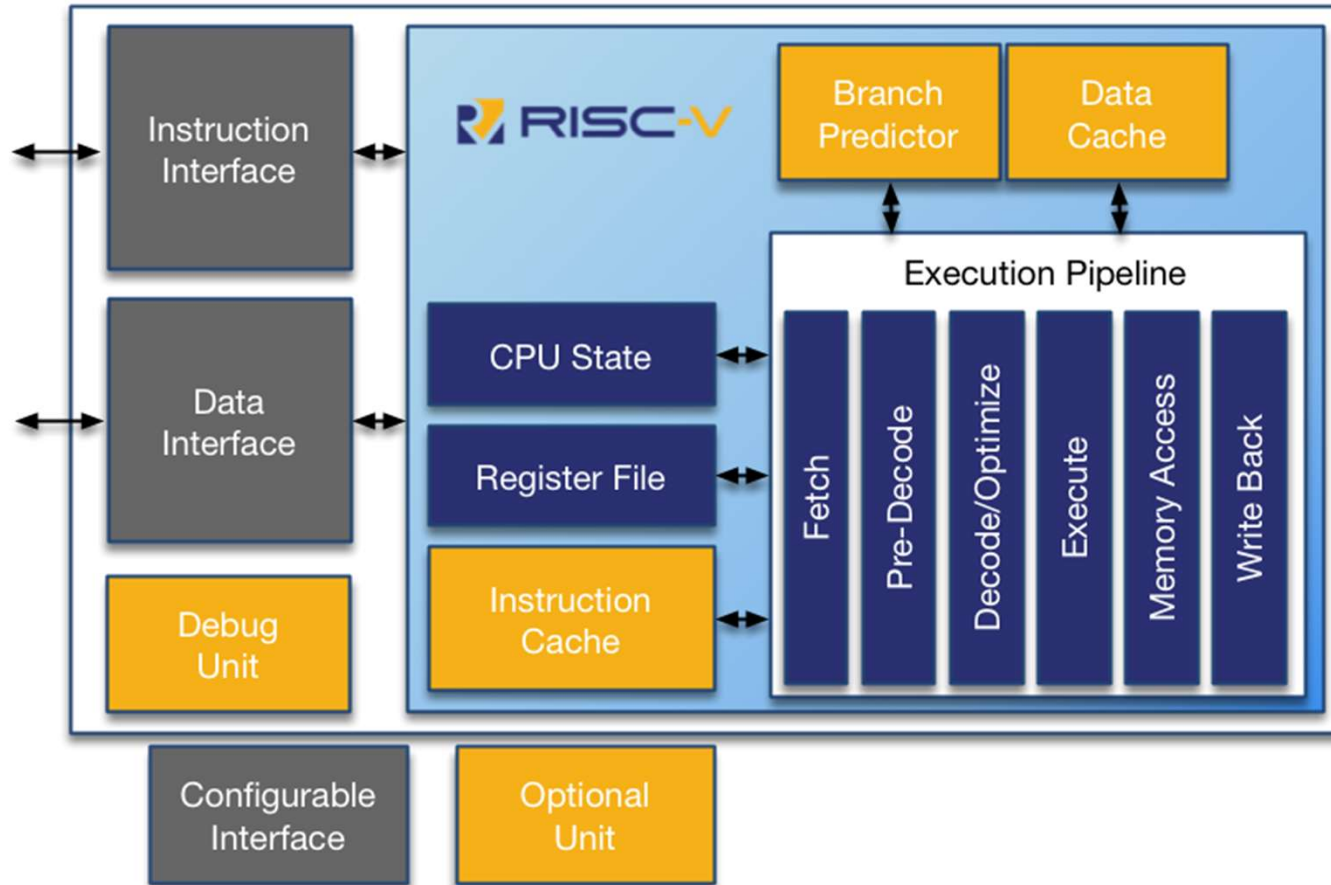




# High Bandwidth Memory

 

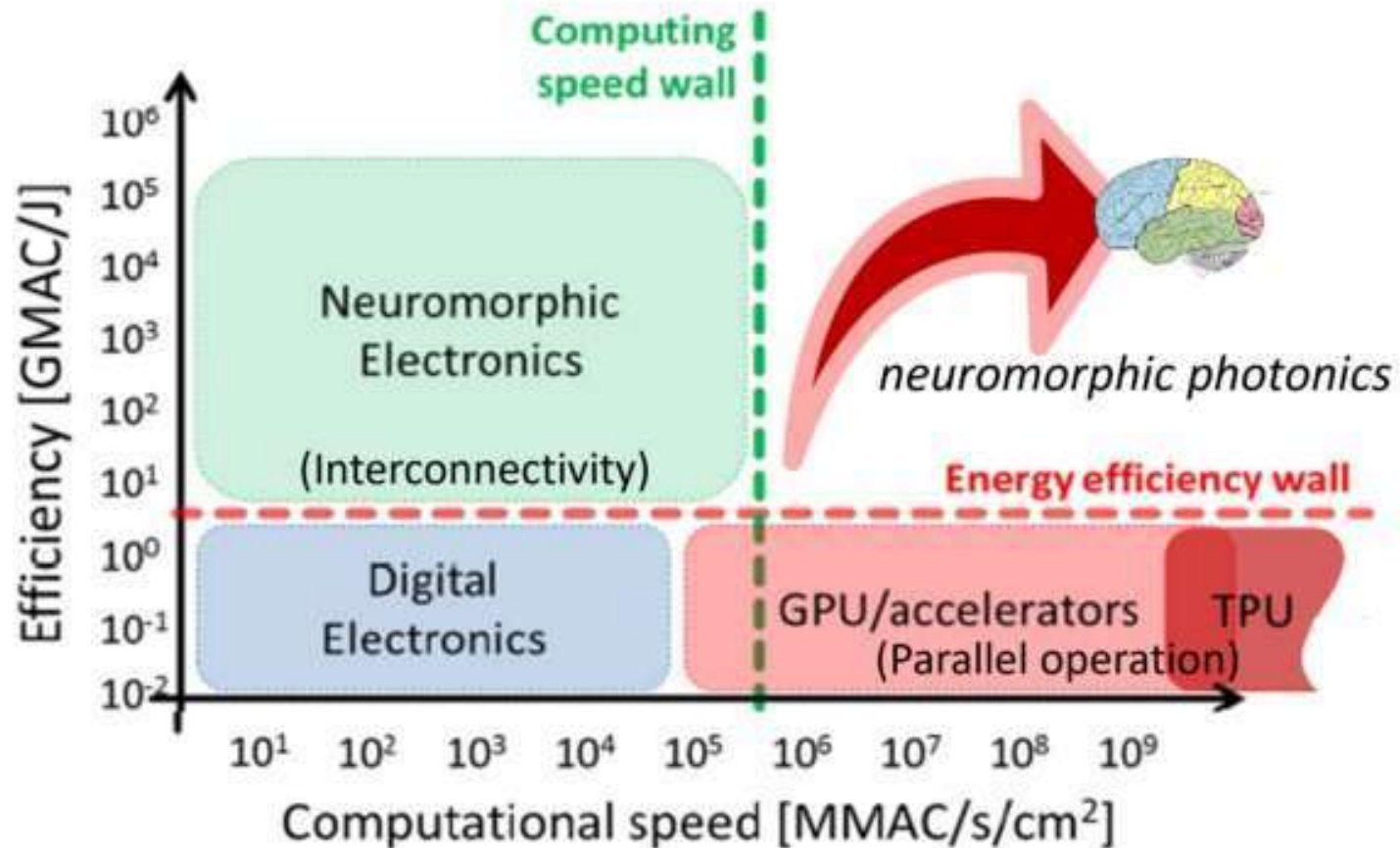
# Changing Architectures, Organizations, Interconnections


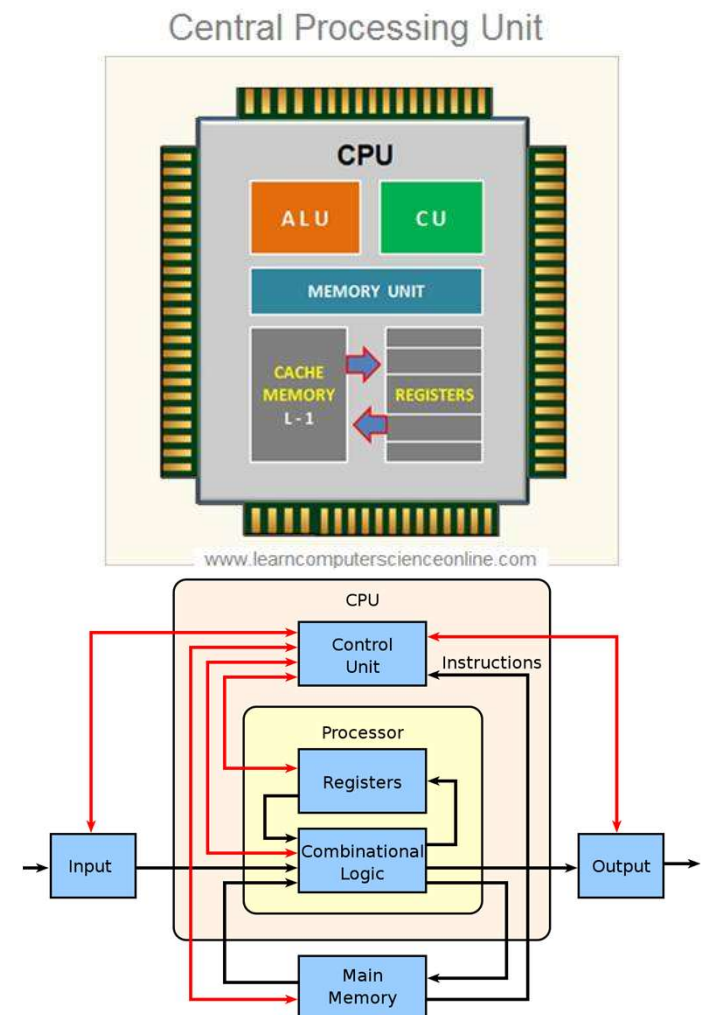
# Main Components inside a Processing Element



- ALU → Specially designed datapath units
- Control Unit → responsible for timing all the events
- Registers / Internal Memory → Program Counter, Data Reg, Inst. Reg,
- Cache
- Buses



# DataPath and ControlPath

 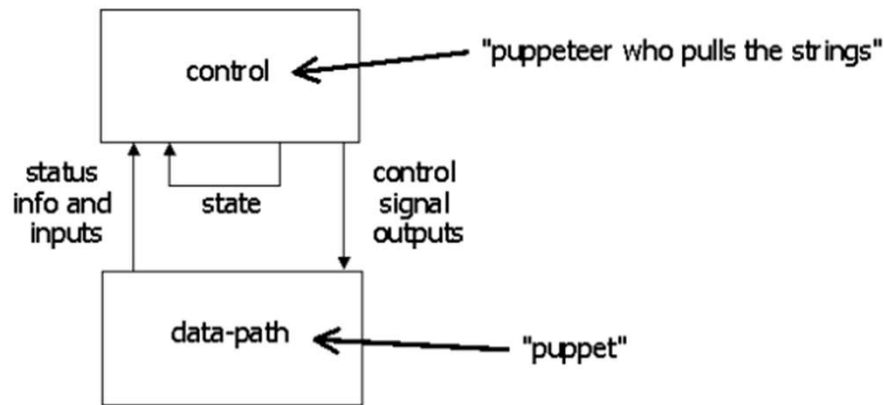
## Data-path and control

- Digital hardware systems = data-path + control
  - datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
  - control: FSM generating sequences of control signals that instructs datapath what to do next




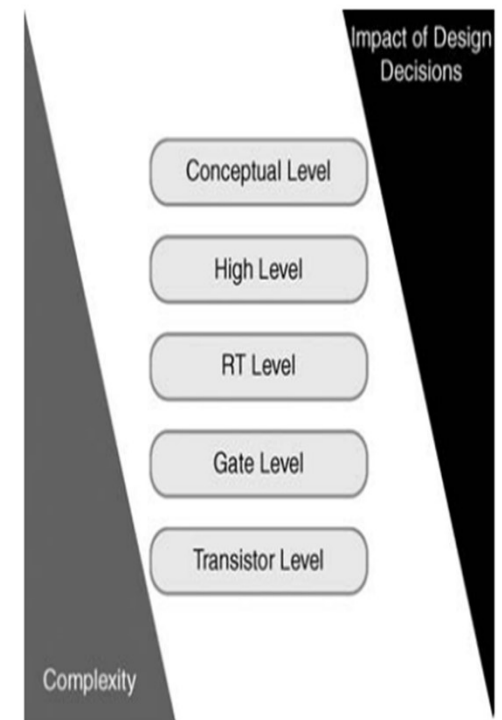
# Four Abstraction Levels

- Switch/Transistor in Triode Level
- Gate Level
- Data Flow Level or RTL Level
  - Expressions, operands and operators characterize this level. Most of the operators used in dataflow modeling are common to software programmers, but there are a few others that are specific to HW design.
- Behavioral or Algo Level
  - The behavioral level is the highest level of abstraction in Verilog.
  - Provides high level language constructs like for, while, repeat, if else and case.
  - Designers with a software programming background already know these constructs.
  - Although the constructs are handy and very powerful, the programmer must know that each construct in RTL Verilog infers hardware.
  - High level constructs are very tempting to use, but the HW consequence of their inclusion must be well understood.
  - For example, for loop to a software programmer suggests a construct that simply repeats a block of code a number of times, but if used in RTL Verilog the code infers multiple copies of the logic in the loop



 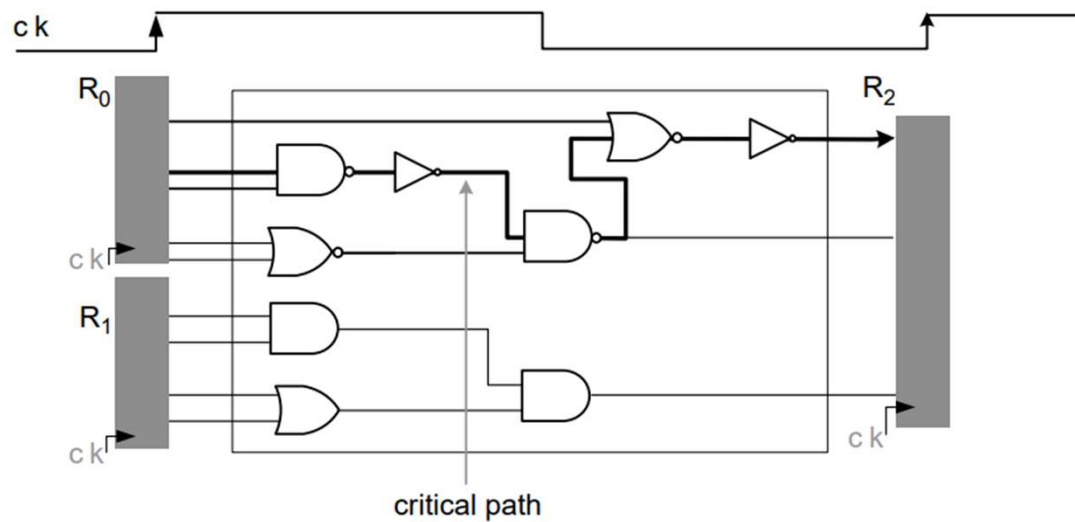
# Register Transfer Level / Partitioning between Combination and Sequential Logic



 
# Combinational Logic

- Output at time  $t$  depends only at input at time  $t$





Combinational

$$\text{Output} = f(\text{In})$$

 

Sequential

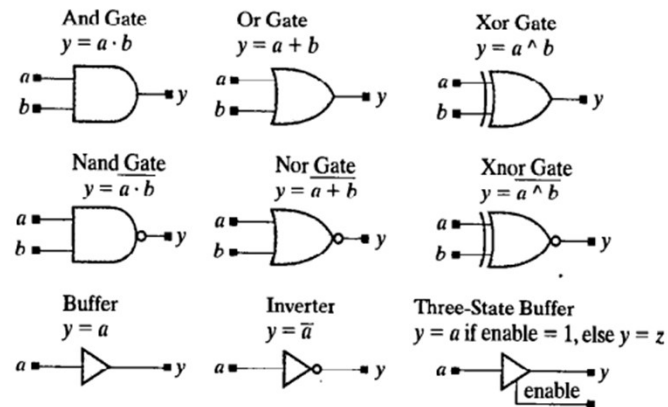 
$$\text{Output} = f(\text{In}, \text{Previous In})$$



| Symbol   | Logic Operation            |
|----------|----------------------------|
| +        | Logic "or"                 |
| ·        | Logical "and"              |
| $\oplus$ | Exclusive "or"             |
| $\wedge$ | Exclusive "or"             |
| '        | Logical negation           |
| -        | Logical negation (overbar) |


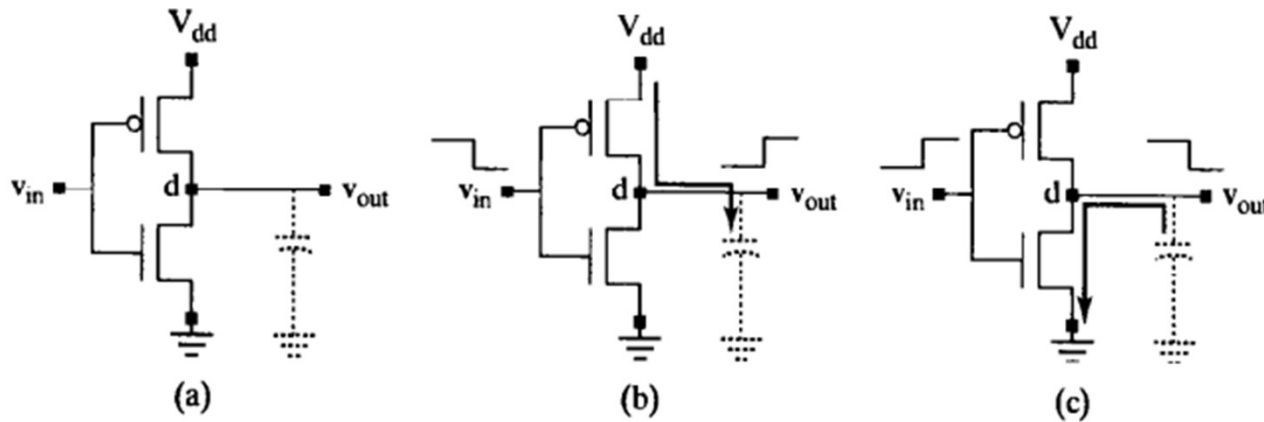
# Looking into the most basic block : Inverter



- Explain:

- Draw input and output and show 50%-50% for  $t_{pLH}$  and also  $R_{on}$  and  $C$
- Assume starting time is zero.

$$v_{out}(t) = (1 - e^{-t/\tau}) V \quad (1.13)$$

The time to reach the 50% point is easily computed as  $t = \ln(2)\tau = 0.69\tau$ . Similarly, it takes  $t = \ln(9)\tau = 2.2\tau$  to get to the 90% point. It is worth memorizing these numbers, as they are extensively used in the rest of the text.



- Explain:

- Why Inversion to start with?
- Why cant NMOS deliver a 1?
- Concept of  $R_{on}$
- Where are capacitors coming from?
- Equation of propagation delay



$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

# Threshold Drops

PUN

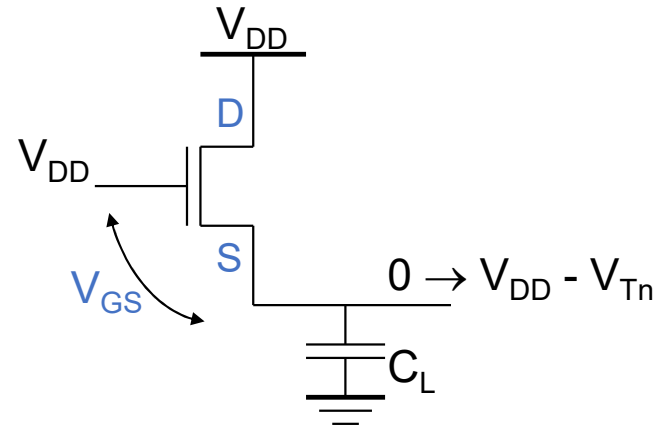 


PDN

 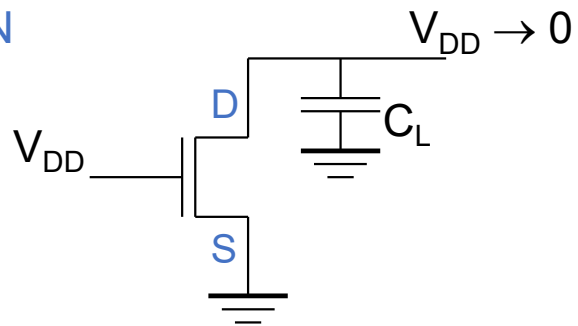
 
# NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal



NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1

  
## PMOS Transistors in Series/Parallel Connection

PMOS switch closes when switch control input is low




PMOS Transistors pass a “strong” 1 but a “weak” 0

# Looking into NAND Gate

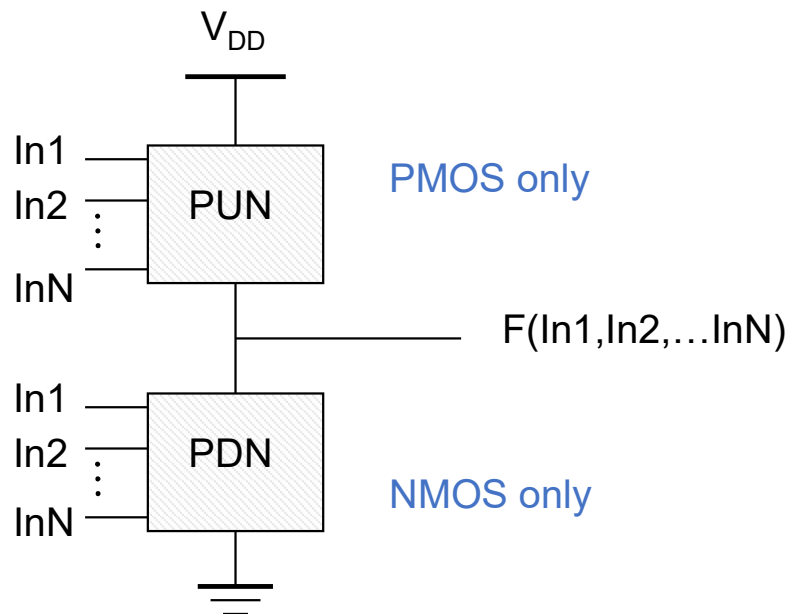


PUN and PDN are **dual** logic networks

# NAND

 

- Explain
  - How Anding is happening
    - Explain we are implementing complement of the required function in the pull down network.
    - We are implementing dual (double bar) with the inverted input in the pull up network
  - Three  $R_{on}$  in series so sizing is critical
    - Relate it to different strengths of gate available for RTL logic

# Complex CMOS Gate

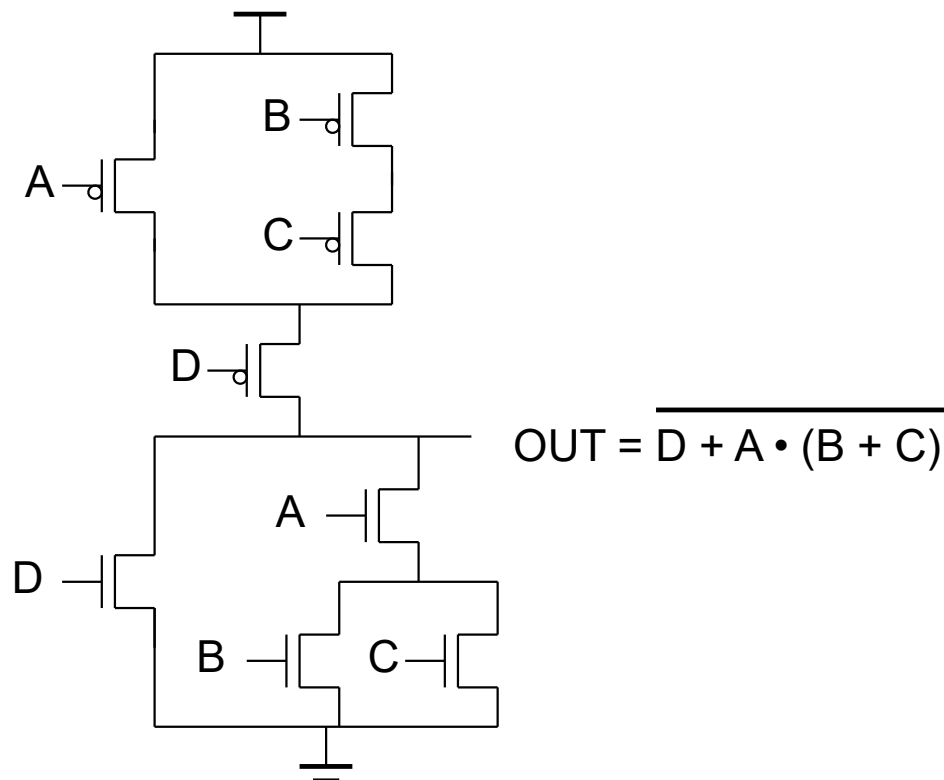

Using complementary CMOS logic, consider the synthesis of a complex CMOS gate whose function is  $F = D + A \cdot (B + C)$ .


The first step in the synthesis of the logic gate is to derive the pull-down network. by using the fact that NMOS devices in series implements the AND function and parallel device implements the OR function.

The next step is to use duality to derive the PUN in a hierarchical fashion


Break network into sub-nets.




# Constructing a Complex Gate

 

(a) pull-down network

 

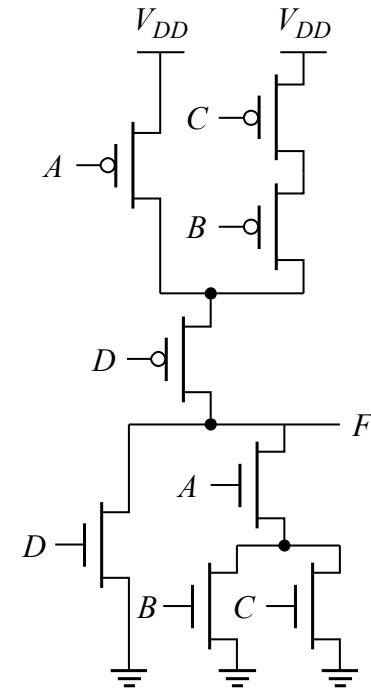(b) Deriving the pull-up network hierarchically by identifying sub-nets




(c) complete gate

# Transistor Sizing a Complex CMOS Gate

Synthesizer will do it for you using your Verilog RTL code and using the timing constraints file!

Must appreciate the automation.

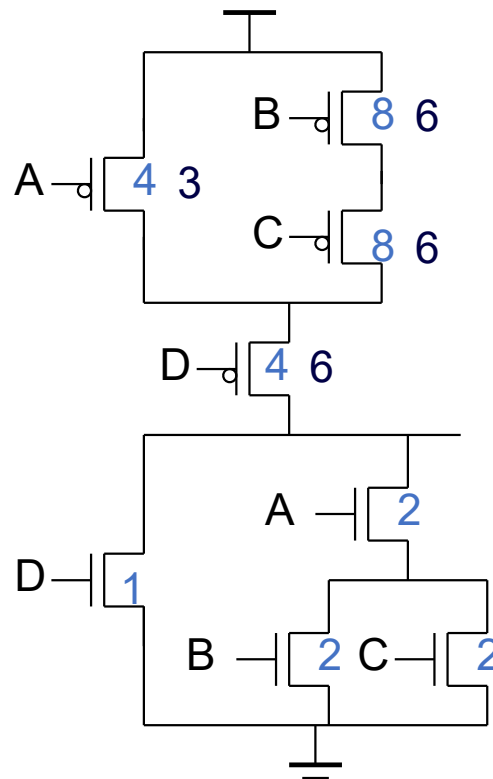But must appreciate the wrong guidance will lead to wrong design.



$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

# Where Does Power Go in CMOS?

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

# Dynamic Power Dissipation

 

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes if internal loading ignored!
- Need to reduce  $C_L$ ,  $V_{dd}$ , and  $f$  to reduce power.

# Short Circuit Currents


 
 
 
 


Figure 5.30 Short-circuit currents during transients.


$$t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} t_s \approx \frac{V_{DD} - 2V_T}{V_{DD}} \times \frac{t_{r(f)}}{0.8} \quad (5.50)$$

# Leakage

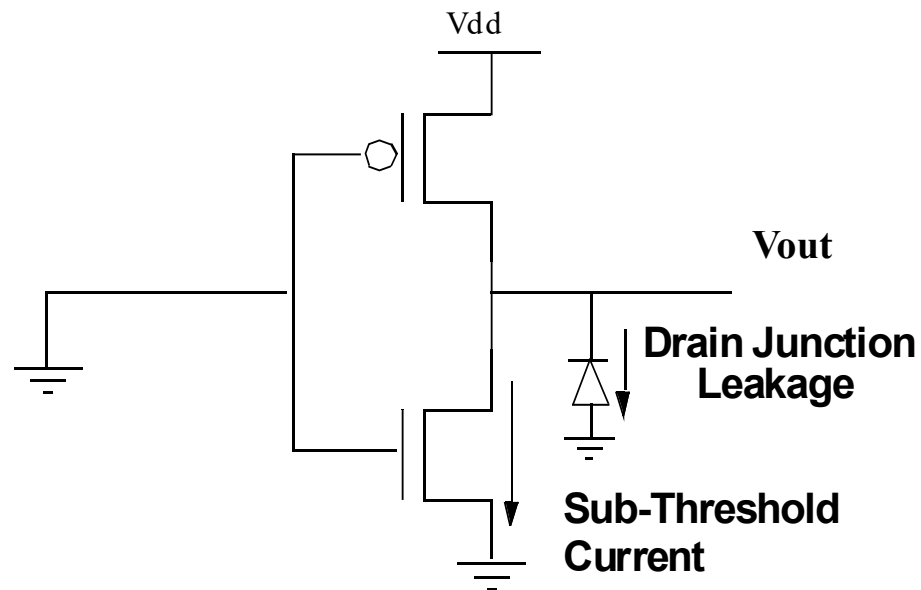

Sub-threshold current one of most compelling issues in low-energy circuit design!

# Reverse-Biased Diode Leakage


 


$$I_{DL} = J_S \times A$$

$J_S = 10\text{-}100 \text{ pA}/\mu\text{m}^2$  at 25 deg C for 0.25 $\mu\text{m}$  CMOS  
 $J_S$  doubles for every 9 deg C!




# Subthreshold Leakage Component

  

- Leakage control is critical for low-voltage operation

# Static Power Consumption

 

$$P_{stat} = P_{(In=1)} \cdot V_{dd} \cdot I_{stat}$$

Wasted energy ...

Should be avoided in almost all cases,  
but could help reducing energy in others (e.g. sense amps)

# Total Power

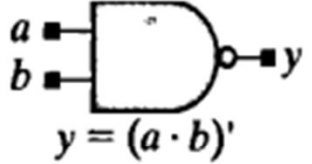
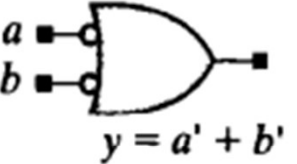
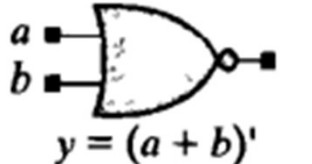

$$P_{tot} = P_{dyn} + P_{dp} + P_{stat} = (C_L V_{DD}^2 + V_{DD} I_{peak} t_s) f_{0 \rightarrow 1} + V_{DD} I_{leak}$$


# Building Blocks for Logic Design

## NAND – NOR Structures

AS we saw, AND and OR are not implemented well in CMOS.

Better to implement SOP using NAND or NOR.

| Gate   | DeMorgan Equivalent  |
|--|--|
| <br>$y = (a \cdot b)'$ | <br>$y = a' + b'$      |
| <br>$y = (a + b)'$    | <br>$y = a' \cdot b'$ |

 



# Multiplexers & Demux

## Multiplexers

$$Y_{out} = a.sel' + b.sel$$

Can be used to implement combinational logic

  Values of Boolean function assigned to input. Select lines used for decoding.



# Encoders and Decoders

Mux and Demux just connect input and output dynamically. Do not change data pattern.

Encoders and Decoders change data-patterns.

Encoders → input word is wider → n inputs and m output ,  $n=2^m$

Decoder → output word is wider

| Input | Output |
|-------|--------|
| 00000 | 000    |
| 00001 | 001    |
| 00010 | 001    |
| 00011 | 010    |
| 00100 | 001    |
| 00101 | 010    |
| 00110 | 010    |
| 00111 | 011    |
| 01000 | 100    |
| 01001 | 010    |
| 01010 | 010    |
| 01011 | 011    |
| 01100 | 010    |
| 01101 | 011    |
| 01110 | 011    |
| 01111 | 100    |

| Input | Output |
|-------|--------|
| 10000 | 001    |
| 10001 | 010    |
| 10010 | 010    |
| 10011 | 011    |
| 10100 | 010    |
| 10101 | 011    |
| 10110 | 011    |
| 10111 | 100    |
| 11000 | 010    |
| 11001 | 011    |
| 11010 | 011    |
| 11011 | 100    |
| 11100 | 011    |
| 11101 | 100    |
| 11110 | 100    |
| 11111 | 101    |

# Priority Encoder

| Input Word | Output Word |
|------------|-------------|
| 1xxxxxxx   | 000         |
| 01xxxxxx   | 001         |
| 001xxxxx   | 010         |
| 0001xxxx   | 011         |
| 00001xxx   | 100         |
| 000001xx   | 101         |
| 0000001x   | 110         |
| 00000001   | 111         |